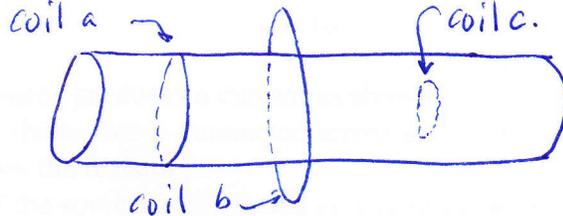


These problems are based on the material in Chapter 30, Inductance.


1. A solenoid is wrapped with wire such that $n = 50,000$ turns/m. The length of the solenoid is 10.0 cm and the radius is 1.0 cm.



a. A coil consisting of 10 turns of wire are wrapped around the solenoid. If the current in the solenoid is I , what is the total flux through the coil? What is the mutual inductance between the solenoid and the coil? If the current in the solenoid goes from $I = 0$ to $I = 5.0$ A in 0.10 sec, what emf is induced in the coils?

b. A second coil, also with 10 turns of wire, has a radius of 2.0 cm and is coaxial with the solenoid. If the current in the solenoid is I , what is the total flux through the coil? What is the mutual inductance between the solenoid and the coil? If the current in the solenoid goes from $I = 0$ to $I = 5.0$ A in 0.10 sec, what emf is induced in the coils.

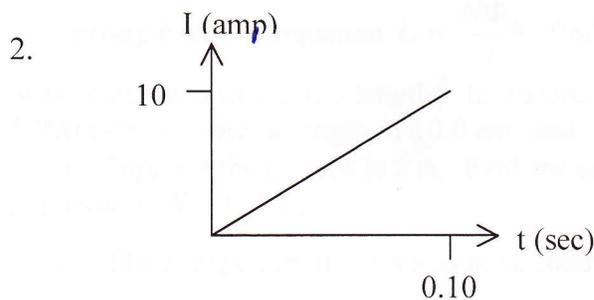
c. A third coil, also with 10 turns of wire, has a radius of 0.50 cm and is also coaxial with the solenoid. If the current in the solenoid is I , what is the total flux through the coil? What is the mutual inductance between the solenoid and the coil? If the current in the solenoid goes from $I = 0$ to $I = 5.0$ A in 0.10 sec, what emf is induced in the coils.



A voltage source produces a current as shown.


a. If the source is connected across a resistor, draw a graph representing the voltage across the resistor.

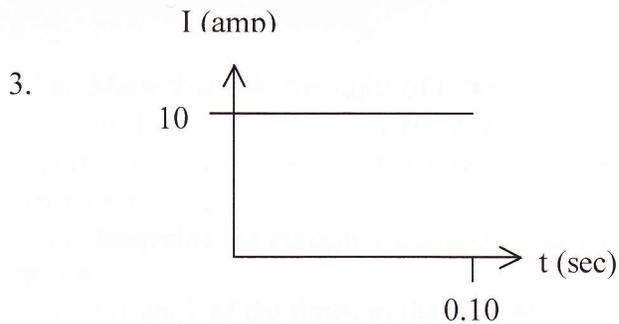b. If the source is connected across an inductor, draw a graph representing the voltage across the inductor.



A voltage source produces a current as shown.

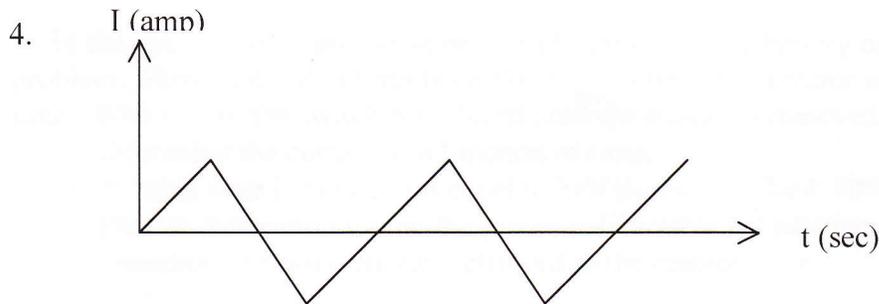- If the source is connected across a resistor, draw a graph representing the voltage across the resistor.
- If the source is connected across an inductor, draw a graph representing the voltage across the inductor.



The graph above represents the current passing through an inductor. Draw a graph representing the voltage across the inductor.

5. Starting from the equation $L = \frac{N\Phi_B}{I}$, find the inductance of an inductor with n turns of wire per m, a radius r , a length l . In particular, find the inductance of an inductor with 5,000 turns of wire, a length of 10.0 cm; and a diameter of 1.0 cm.


a. Suppose the current is 5 A. Find the energy stored in the inductor using the expression $W = \frac{1}{2} LI^2$.

b. The energy density in a magnetic field is $\frac{1}{2\mu_0} B^2$. Use this expression to verify the energy you determined in part a.

6. It has been proposed to use large inductors to store electrical energy.


- How much energy does it take to run a 100-W light bulb for 24 hours?
- If the energy is stored in a magnetic field of 5.0 T, how large a volume is needed?
- If the energy is stored in an inductor carrying 50 A of current, what is the inductance needed?

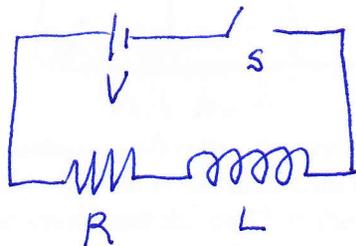7. a. Show that L/R has units of time, when L is in Henrys and R is in ohms.
 b. In the circuit below is a $10\ \Omega$ resistor, a $5.0\ \text{H}$ inductor, and a $10\ \text{V}$ battery. Initially there is no current. Find the current as a function of time starting when the switch S is closed.
 c. Determine the current $0.0\ \text{sec}$, $0.5\ \text{sec}$, $1.0\ \text{sec}$, and $3600\ \text{sec}$ after the switch is closed.
 d. For each of the times in the previous problem, verify that the voltage across the resistor plus the voltage across the inductor = $10\ \text{V}$.



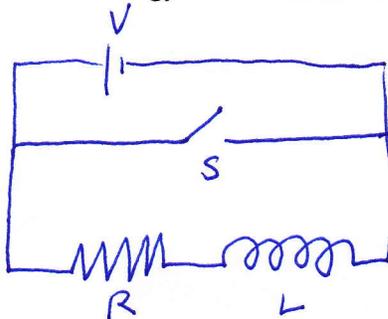8. In the circuit shown are the same resistor, inductor, and battery of the previous problem. However, current has been flowing through the inductor and resistor for a long time. When $t = 0$, the switch S is closed (and the battery is removed from the circuit).
 a. Determine the current as a function of time.
 b. At what time is the current equal to half its initial value? 10% of its initial value?
 c. Find an expression giving the power delivered to the resistor as a function of time.
 d. Determine the total energy delivered to the resistor from

$energy = \int_0^{\infty} power\ dt$. Show that this energy is the same as the initial energy stored in the inductor.



9. In the circuit shown is a $2\ \mu\text{F}$ capacitor and a $0.50\ \text{H}$ inductor. Initially, the switch is open, and the charge on the capacitor is $10.0\ \text{V}$.

- a. When the switch is closed, what is the frequency of oscillation?
 b. What is the initial energy in the capacitor?
 c. Find the energy of the inductor as a function of time. Find the maximum current in the inductor. Show that the maximum energy stored in the inductor equals the initial energy stored in the capacitor.

